

## Feedback in Amplifier

→ When a part or fraction of o/p is combined to the input, is feedback.


→ Positive feedback causes excessive distortion and instability. However, because of its capability of increasing the power of the original signal it is used in oscillator circuits.

→ When the feedback voltage is so applied as to weaken the i/p signal, it is called negative feedback.


\* Negative feedback weakens the i/p signal, reduces the amplifier gain but it has numerous advantages [such as gain stability, reduction in non-linear distortion, reduction in noise, increase in B.W. or improvement in freq. response, increase in input impedance and decrease in output impedance]

feedback n/w :-

### ① Voltage Series feedback

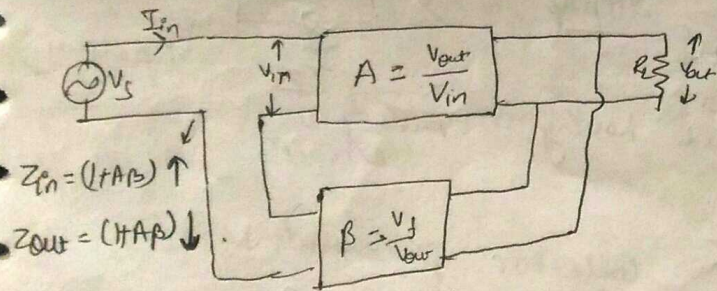


### ② Voltage - Shunt feedback

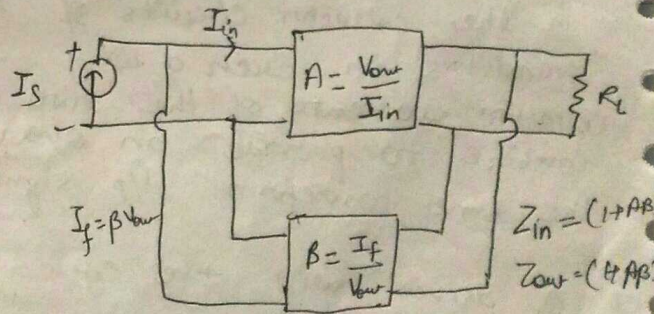


Voltage feedback tends to reduce the output impedance

Current " " " increase " " "

### Current Series

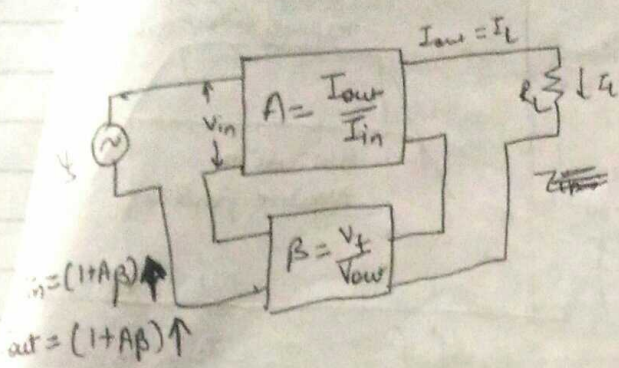

### Current Shunt

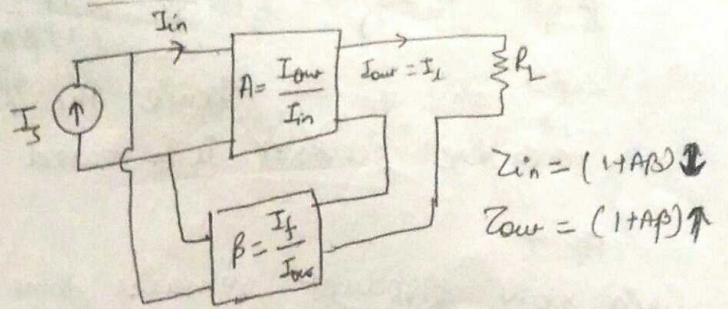

Negative feedback =  $\frac{A}{1 + \beta A}$       positive feedback =  $\frac{A}{1 - \beta A}$

Every amplifier stage introduces a phase shift of  $180^\circ$ .

- ①  $(1 - \beta A) < 1$ , Gain  $\uparrow$  but reduces stability and  $\uparrow$  distortion
- ②  $(1 - \beta A) = 0$ , Gain  $\neq \infty$  possible when  $\phi$  is zero
- ③  $(1 - \beta A) > 1$ , Gain  $= \downarrow$  (Same as -ve feedback)

### Advantage of Negative feedback :-

① Gain stability :-  $A_f = \frac{A}{1 + \beta A}$

so  $A_f$  is independent of internal gain if  $\beta A \gg 1$ ,  $A_f = \frac{1}{\beta}$   
 $\beta$  which in turn depends on passive elements depends on resistors  
 resistors remain fairly constant so the gain is stabilised.

- ② Reduced Non-linear Distortion :-  $\downarrow$  by  $(1 + \beta A)$
- ③ Noise =  $\downarrow$  by  $(1 + \beta A)$
- ④ increased BW =  $\uparrow$  by  $(1 + \beta A)$
- ⑤ increased  $\uparrow$  p impedance =  $\uparrow$  by  $(1 + \beta A)$
- ⑥ Decrease o/p " =  $\downarrow$  by  $(1 + \beta A)$

Reduction in Noise with Negative feedback :-  $(1 + \beta A)$  factor reduces the noise

Input Impedance :-  $Z_{inf} = Z_{in}(1 + \beta A)$


Output Impedance :-  $Z_{outf} = \frac{Z_{out}}{(1 + \beta A)}$

Negative feedback on BW :-  $f_1' = \frac{f_1}{(1 + \beta A)}$        $f_2' = f_2(1 + \beta A)$

$$BW_f = f_2' - f_1' = f_2(1+A\beta) - \frac{f_1}{(1+\beta A)}$$

$f_2' > f_2$  and  $f_1' < f_1$ , hence the BW with negative feedback is increased

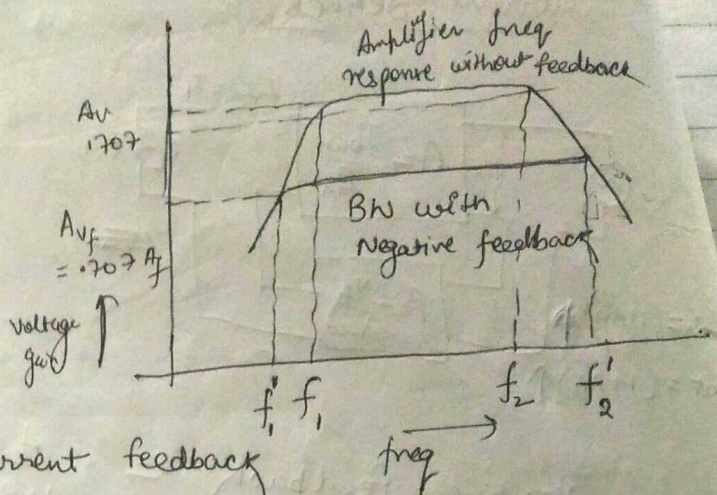$BW_f \approx$   
Gain  $\times$  BW product remains same




Emitter follower :- It is negative current feedback

- ② large i/p impedance & a small output impedance
- ③ voltage gain  $\approx 1$
- ④ output voltage tends to be in phase with the i/p voltage, hence the term follower.
- ⑤ The emitter resistance  $R_E$  itself acts as the load and the ac output voltage  $V_{out}$  is taken across it.

$V_{out} = I_E R_E$  across the  $R_E$

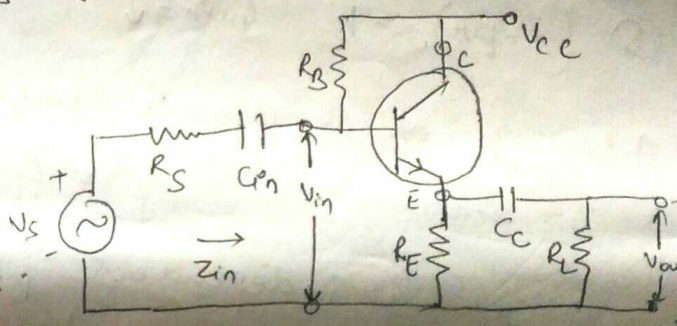This voltage opposes the ac signal voltage  $V_s$  as it is in phase opposition to  $V_s$ . Thus it provides -ve current feedback.



\*  $V_{out}$  feedback to the i/p is proportional to  $I_E$  hence this ckt is called a negative current feedback circuit.

Advantage :- \* High i/p impedance & Low o/p impedance so can be used for impedance matching (impedance transformer).

- \* Because of 100% feedback, o/p is distortionless & BW is very large.
- \*  $\uparrow$  current gain &  $\uparrow$  power gain
- \* o/p & i/p ac voltages are in phase,

Application :- It is capable of transferring maximum power from high impedance source to low impedance load.

- \* It is called a buffer amp.
- \* Provide better freq. response than transformer.

## Negative feedback

- 1) Negative feedback is used in voltage amplifier.
- 2) The feedback network is always resistive and network act as voltage divider.

Features :- (i) voltage gain decreases :-

$$A_{VF} = \frac{A_V}{1 + KA_V}$$

(ii) stability increase :-

$$A_{VF} = \frac{A_V}{1 + KA_V}$$

if  $KA_V \gg 1$

$$A_{VF} = \frac{A_V}{KA_V} \cong \frac{1}{K}$$

$\left\{ \begin{array}{l} A_{VF} \text{ depends on} \\ \text{only } K \text{ not in } A_V. \\ K \text{ is not dependent} \\ \text{on } h \text{ parameter.} \\ \text{and } h \text{ parameter depends} \\ \text{on temp.} \end{array} \right.$

(iii) Lower cut-off frequencies decreases :-

$$F_1' = \frac{F_1}{1 + KA_V}$$

(iv) Upper cut-off frequencies increases :-

$$F_2' = F_2 (1 + KA_V)$$

(v) Bandwidth increases :-  $BW' = BW(1 + KA_V)$

(vi) Gain bandwidth remain constant.

(vii) Noise decreases :-

$$N' = \frac{N}{1 + KA_V}$$

(viii) Distortion decreases :-

$$D' = \frac{D}{1 + KA_V}$$

(ix) Input impedance may increase or decreases :-  $\rightarrow$  Best

$$Z_{inF} = Z_{in} (1 + KA_V) \text{ for } \left\{ \begin{array}{l} \text{Voltage series} \\ \text{Current series} \end{array} \right\} \text{ Increase}$$

$$Z_{inF} = \frac{Z_{in}}{1 + KA_V} \text{ for } \left\{ \begin{array}{l} \text{Voltage shunt} \\ \text{Current shunt} \end{array} \right\} \text{ decrease}$$

(x) output impedance :-

$$Z_{oF} = Z_o (1 + KA_V) \text{ for } \left\{ \begin{array}{l} \text{Current series} \\ \text{Current shunt} \end{array} \right\} \text{ Increase}$$

$$Z_{oF} = \frac{Z_o}{1 + KA_V} \text{ for } \left\{ \begin{array}{l} \text{Voltage series} \\ \text{Voltage shunt} \end{array} \right\} \text{ Decrease}$$

## Various feedback configurations

1) Voltage - series :- [series - shunt]  
I/O O/P

{ best configuration }

(i)  $Z_{in} \uparrow$  (ii)  $Z_{out} \downarrow$

e.g. Common collector / emitter follower

2) Voltage - shunt :- [shunt - shunt]  
I/O O/P

(i)  $Z_{in} \downarrow$  (ii)  $Z_{out} \downarrow$

e.g. fixed biased

3) Current - series :- [series - series]

(i)  $Z_{in} \uparrow$  (ii)  $Z_{out} \uparrow$

e.g. common emitter with  $R_E$

4) Current - shunt :- [shunt - series]

(i)  $Z_{in} \downarrow$  (ii)  $Z_{out} \uparrow$

{ worst case }

## Features of Negative feedback:-

1. voltage gain is decreases:-

$$A_{vf} = \frac{A_v}{1 + K A_v}$$

2. Stability increases:-

$$A_{vf} = \frac{A_v}{1 + K A_v}$$

if  $K A_v \gg 1$

$$A_{vf} = \frac{A_v}{K A_v} \approx \frac{1}{K}$$

$A_{vf}$  depends on only  $K$  not in  $A_v$ .  
 $K$  is not dependent of  $h$  parameter.  
[ $h$  parameter depends on temp.,.]

The overall voltage gain  $A_{vf}$  depends only upon the externally connected feedback  $h_{11}$  and does not depend upon the voltage gain of the original amplifier. Since  $A_v$  depends upon the  $h$  parameters which are temp. dependent therefore insensitive of the variation in the temp. the overall voltage gain remains almost constt., hence the thermal stability of the overall amplifier increases.

3. Lower cut off frequencies is decreases:—

$$f_1' = \frac{f_1}{1+K_{AV}}$$

4. Upper cutoff frequencies is increases:—

$$f_2' = f_2 [1+K_{AV}]$$

5. Bandwidth increases:—

$$BW' = BW [1+K_{AV}]$$

6. GBW - remains constt.

$$GBW' = A_{vf} \times BW'$$

$$= \frac{A_v}{1+K_{AV}} \times BW [1+K_{AV}]$$

$$GBW' = A_v \times BW = GBW$$

7. noise decreases:—

$$noise' = \frac{N}{1+K_{AV}}$$


$$N' = \frac{N}{1+K_{AV}}$$

N = noise

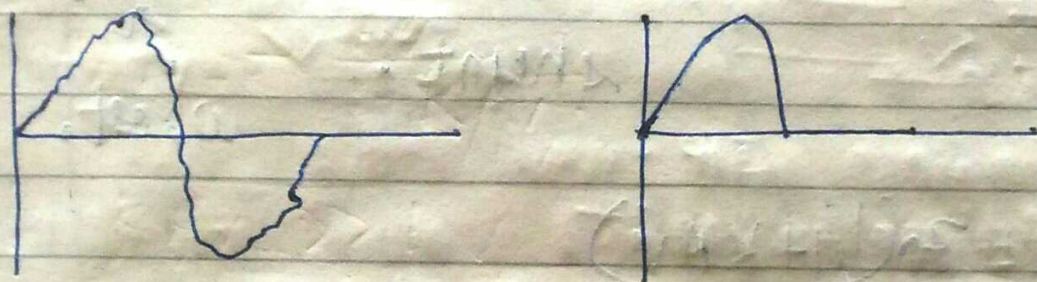8. Distortion decreases:-


$$DI = \frac{D}{1 + KAV}$$

\* fundamental difference b/w noise and distortion:-



distortion - some portion of sig is distorted or clipped.

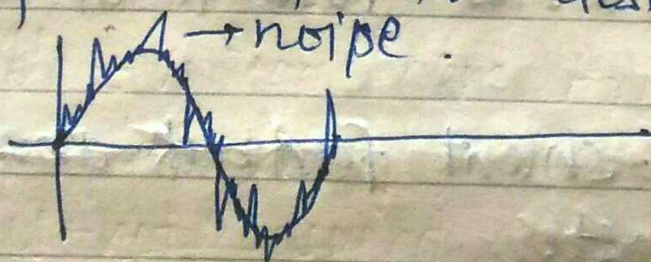noise = undesired signal which are superimposed with the desired signal.



9. Z<sub>in</sub> impedance may increase or decrease:-

$$Z_{in} = Z_{in}(1 + KAV)$$

Voltage-series  
Current series

$Z_{in} \uparrow$

$Z_{in}$  will be  $\downarrow$ :-



voltage shunt and current shunt type arrangement.

10) o/p impedance:—  
may increase or decrease.


$Z_{out f} = Z_{of} = Z_o(1 + K_{AV})$  = due to current-series and current-shunt.   
↑  
worst.

$Z_{out f} = Z_o(1 + K_{AV})$   
= voltage series  
= voltage shunt.

\* From IIP and OIP impedance point of view:—

- 1) Voltage-series feedback arrangement is best.
- 2) Current-shunt feedback arrangement is the worst.
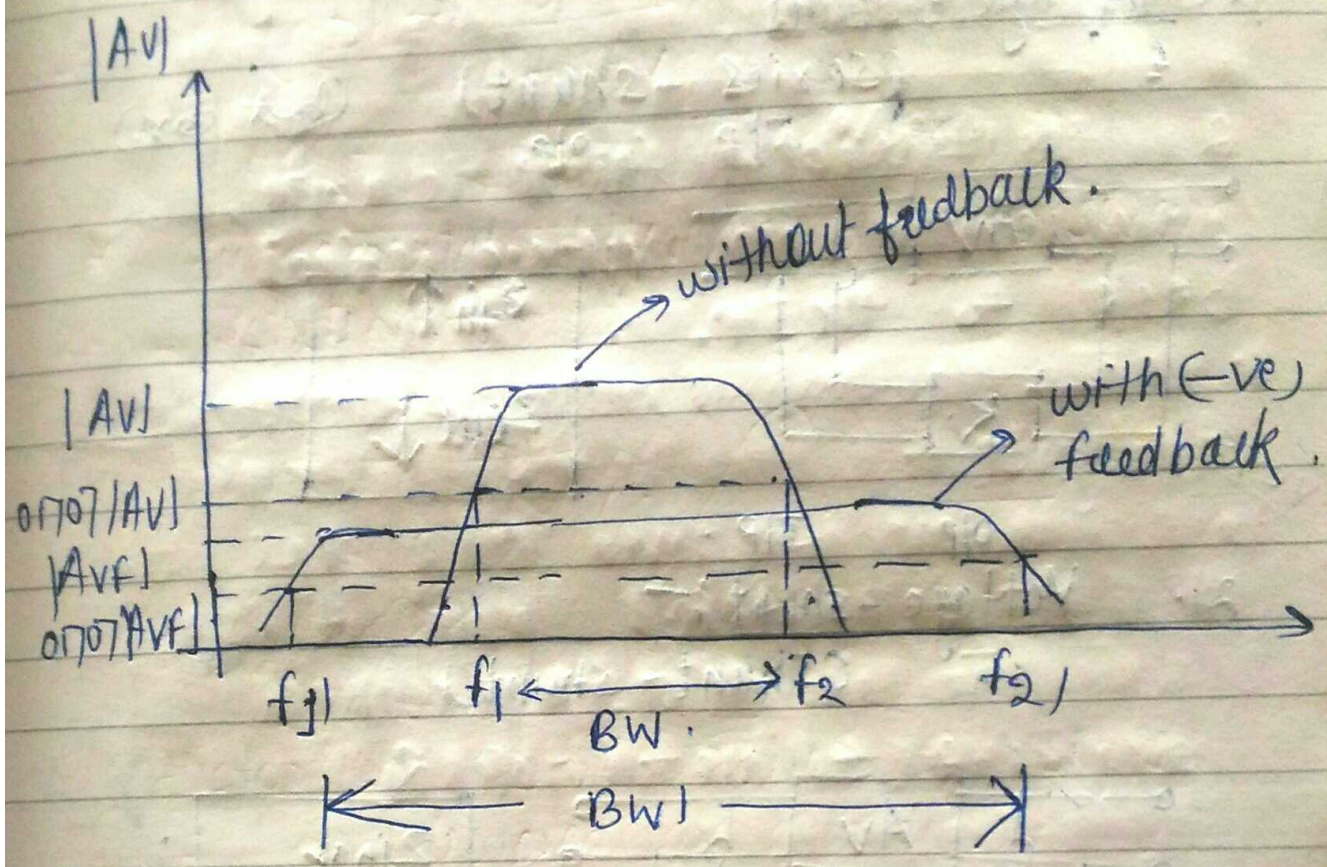
## Frequency response of the feedback amplifiers :-



Hence by using  $-ve$  feedback :-

- 1) voltage gain decreases.
- 2) Lower cutoff frequency  $\downarrow$
- 3) Upper  $\uparrow$
- 4) BW  $\uparrow$
- 5) gain band width product before and after negative feedback remains constt.
- 6) Hence by using appropriate cascading and negative feedback we can obtain the desired value of the voltage gain as well as necessary bandwidth.

Let  $f_2^{(n)}$  be the upper 3-dB freq. for the complete cascade amplifier.  
 If all stages are identical.  $f_2 = f_2' = f_2'' = f_2''' \dots = f_2^{(n)}$

$$\frac{f_2^{(n)}}{f_2} = \sqrt{2^{1/n} - 1}$$

If  $f_1$  be the lower 3-dB freq. of each of the  $n$  identical non-interacting cascade stages.


$$\frac{f_1^{(n)}}{f_1} = \frac{1}{\sqrt{2^{1/n} - 1}}$$

So for cascade amp<sup>r</sup> 3-dB BW is reduced.
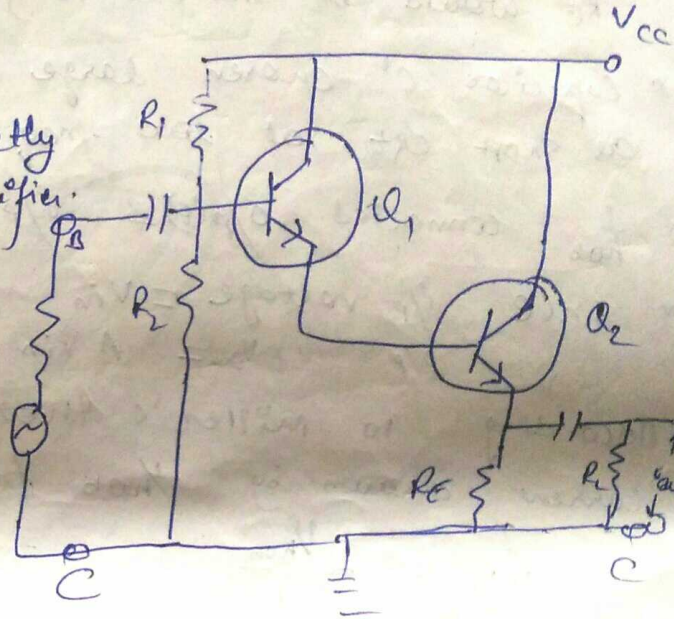
### Darlington Amplifier:-

- In this emitter of one amplifier is directly joined with base of the other amplifier.
- $I_E$  of first transistor becomes the  $I_B$  of the second transistor.
- Two cascade emitter follower (CC) with  $\infty R_E$  resistance of 1<sup>st</sup> stage
- Current gain  $A_i \approx \beta_1 \beta_2$

$$= (1 + \beta_1)(1 + \beta_2) \approx \beta_1 \beta_2$$




i/p impedance  $\rightarrow$  of the darlington Amplifier is higher than a single amplifier

o/p impedance - is lower than a single amp<sup>r</sup>.

Merits:- It provides excellent characteristics of high input impedance with low o/p impedance and high current gain, all desirable characteristics for a current gain amplifier.


Application:- used high gain operational amp<sup>r</sup> which depends on very high i/p impedance for its operation as an integrator or summing amp<sup>r</sup>.

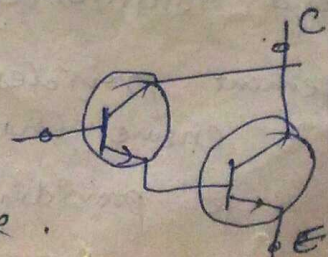This is Darlington transistor  $\rightarrow$  with high current gain & high i/p impedance.



Bootstrapped Darlington ckt:- for Darlington ckt the input resistance is limited ( $r_{in} \approx 2M\Omega$ ) b/w base & collector the i/p resistance can be largely increased by bootstrapping the darlington ckt  $\rightarrow$  through the addition of capacitor  $C'$  b/w I<sup>st</sup> collector terminal  $C_1$  & II<sup>nd</sup> emitter terminal  $E_2$

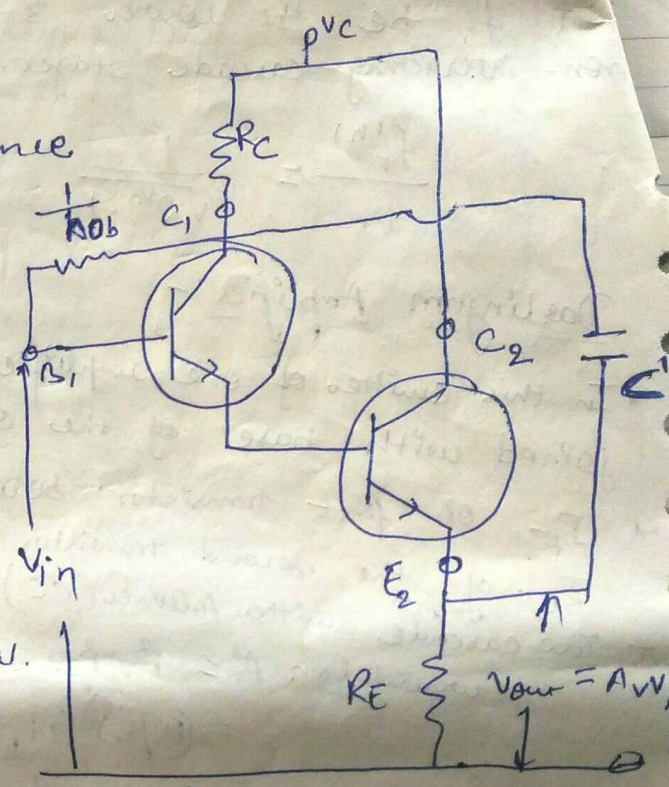- \* Consider a self bias ckt
- \*  $R_C$  is essential because in its absence  $R_E$  would be shorted to ground.
- \* Capacitor  $C'$  chosen large to act as short ckt at low freq.
- \*  $r_{in}$  connected o/p (E) & i/p (B).
- \* since i/p voltage =  $V_{in}$   
o/p  $\Rightarrow V_{out} = A V_{in}$



According to Miller's theorem.  
current drawn by  $r_{in}$  from i/p signal.

$$R_{eff} = \frac{r_{in}}{(1-AV)}$$

As  $AV \rightarrow 1$   $R_{eff} \rightarrow \infty$  (extremely large)  
is called bootstrapping.

i/p impedance  $R_i = \frac{h_{ie}}{(1-AV)}$

$$R_{in} = h_{ie1} h_{ie2} R_{eff}$$

$$R_{eff} = R_C \parallel R_E$$

Cascade Amplifier:- has one transistor on top of (in series) with another.

first transistor  $Q_1 \rightarrow$  CE in input stage while the circuit of second transistor  $Q_2 \rightarrow$  CB in output stage

- \* Arrangement provides high i/p impedance with low voltage gain to ensure that the i/p miller capacitance is minimum
- \* CB stage providing good high freq operation.

for DC condition.

is CE configuration:-

$I_{E1}$  is set by  $V_{E1}$  &  $R_4$

$I_{E1} \approx I_{C1}$  &  $I_{E1} \approx I_{E2}$

$I_{C2} \approx I_{E1}$ . This current remains const. regardless of the level of  $V_{B2}$

i/p impedance of emitter of transistor  $Q_2$


voltage gain of 1st  $A_{V1} = -\frac{h_{fe}}{h_{ie}} \times (Z_{in \text{ to } Q_2})$

$= -\frac{h_{fe}}{h_{ie}} \left[ \frac{h_{ie}}{1+h_{fe}} \right] = -1$

voltage gain of 2nd

$A_{V2} = \frac{h_{fb} \times (R_5 || R_L)}{h_{ib}}$

overall =  $-\frac{h_{fb}(R_5 || R_L)}{h_{ie}}$

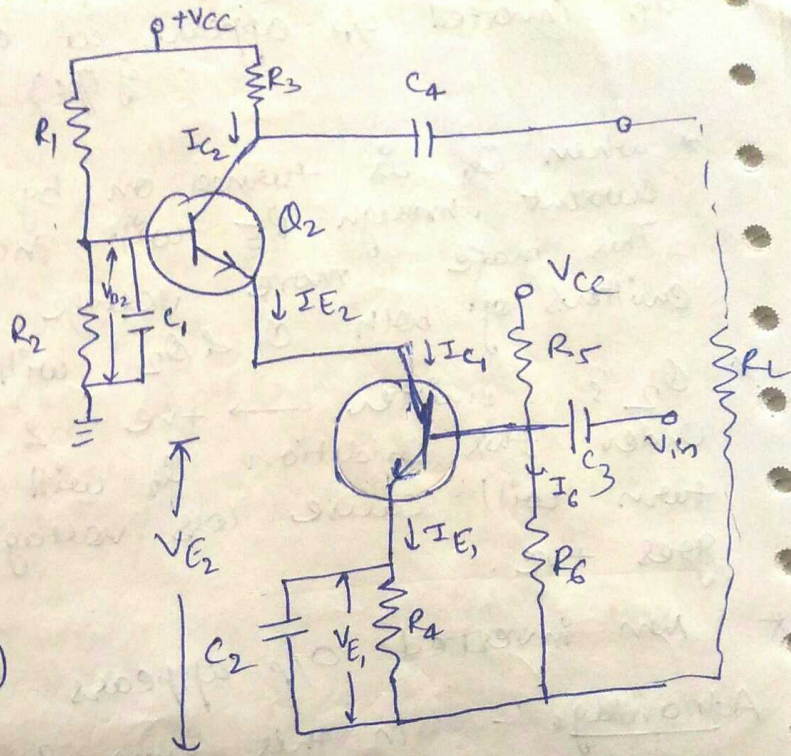

\* Differential Amplifier:-

Give difference b/w the two i/p signals.

\* i/p is applied different-different base terminal

\* ~~of~~ emitters of each are connected with a common emitter resistor

so that the two o/p terminals.  $V_{out1}$  &  $V_{out2}$  are affected by either or both i/p signals.

\* when i/p signal drives transistor  $Q_1$ , there will be more voltage drop across  $R_{C1}$  and therefore collector  $Q_1$  will be less +ve.

\* when i/p signal is -ve it will turn off the transistor and so voltage drop across  $R_{C1}$  will be negligible and collector  $Q_1$  will be more +ve

