

## Tuned Amplifier


Amplifier  $\leftarrow$  DC amplifier (from zero to about 10Hz)  
 Audio amplifier (20Hz to 20KHz)  
 Radio " (a few KHz to hundred of MHz)

\* Some times selection of a desired freq. or a narrow band of frequencies for amplification is our need, such as in radio/TV the receiver is required to pick up and amplify the desired radio freq. while rejecting all other. Amplifier, amplifying a signal of specific freq. or narrow band of frequencies is known as tuned Amplifier.

\* Employed for amplification of high or radio freq. signals and can't used for amplification of audio-freq. signals, because :-

- ① Tuned amp<sup>r</sup> select & amplifies a single freq. while AF are mixtures of frequencies in the freq. range of (20Hz - 20KHz)
- ② for amplification of low freq. signals large valued, inductor & capacitors are required  $f_r = \frac{1}{2\pi\sqrt{LC}}$

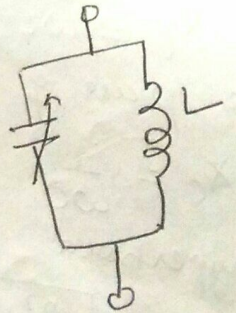
Tuned The centre of this freq. band is the resonant freq. of the tuned ckt.



Resonant L-C circuit as a load provides high impedance and so the tuned transistor amplifier can provide high gain because gain of a transistor amplifier depends on the value of its load impedance. only narrow band of frequencies around the resonant freq.  $f_r$  would be amplified well while other frequencies would be discriminated.

Resonant ckt :-

① Series resonant ckt :-

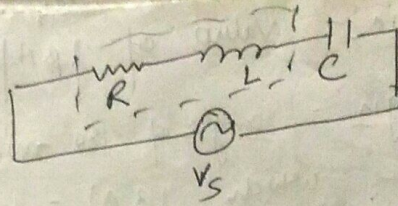

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

② when  $X_L = X_C$

③  $Z = R$

④ Current flowing through the ckt is maximum and in phase with the applied voltage.  $I = V/R$ .

⑤  $V_C = V_L$  but opposite in phase

⑥ power factor = 1

⑦ power expended =  $VI$  watts

The ckt is said to be in resonance and the freq. at which it occurs is known as resonant freq.

$$\omega L = \frac{1}{\omega C} \Rightarrow$$

$$\omega^2 = \frac{1}{LC} = (2\pi f)^2 = \frac{1}{LC} \Rightarrow 2\pi f = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Since voltage is max. So it is called voltage resonance.

The series resonance is called an acceptor circuit because such a circuit accepts currents at one particular freq. but rejects current of other frequencies.

$X_L = \omega L$  so represented by straight line passing through the origin.

$X_C = \frac{1}{\omega C}$  represented by rectangular hyperbola



$Z = \sqrt{R^2 + (X_L - X_C)^2}$  is minimum at resonant

freq ( $f_r$ )

\* At freq. lower than resonant freq.  $f_r$  the impedance  $Z$  is large and capacitive as  $X_C > X_L$  & power factor is leading

\* At higher freq. than  $f_r$   $Z$  is again large but inductive  $X_L > X_C$  and power factor is lagging. At resonance Power factor = 1

Resonance curve :-

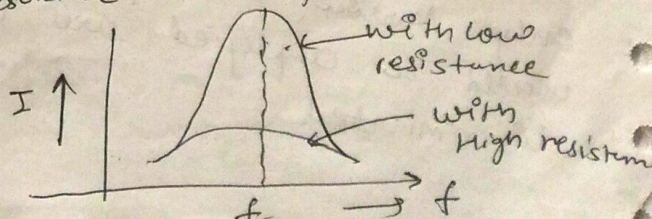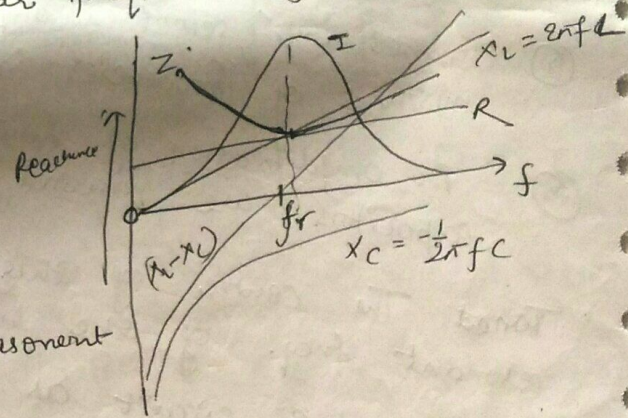

selectivity and B.W. :-  $\star$  low resistance circuit the resonance curve is sharply peaked and such a circuit is said to be sharply - resonant or highly selective.

$\star$  High resistance ckt have flat resonance curve and is said to have poor selectivity.

$$\text{Actual power } P = I^2 R = \left(\frac{I_{\max}}{\sqrt{2}}\right)^2 R = \frac{I_{\max}^2}{2} R = \frac{1}{2} P_{\max}$$

$$P = \frac{1}{2} \times \text{Power i/p at resonance}$$

At half power points :-

① Current  $\frac{I_{\max}}{\sqrt{2}}$

② Impedance  $= \sqrt{2} R = \sqrt{2} Z_{\min}$

③  $P_1 = P_2 = \frac{P_{\max}}{2}$

④ phase angle  $\phi = \pm 45^\circ$  or  $\frac{\pi}{4}$  radians

Quality factor :- defined by :-

① It may be given as the voltage magnification that the circuit produces at resonance.

Supply voltage  $V = I_{\max} R$ , voltage across inductance or capacitance  $= I_{\max} X_L = I_{\max} X_C$

$$\text{Voltage magnification} = \frac{I_{\max} X_L}{I_{\max} R} = \frac{X_L}{R} = \frac{\omega L}{R} = \frac{1}{\omega R C}$$

$$Q = \frac{\omega L}{R} = \frac{2\pi f_r L}{R} = \frac{2\pi L}{R} \frac{1}{2\pi \sqrt{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

② Q-factor of a coil is a measure of its efficiency of energy storage when it carries ac.

$$Q = 2\pi \times \frac{\text{max energy stored}}{\text{Energy dissipation per cycle}} = \frac{2\pi \times \frac{1}{2} L I_{\max}^2}{\frac{I_{\max}^2 R}{2} / f_r}$$


$$= \frac{2\pi L \times f_r}{R} = \frac{\omega L}{R}$$

③ higher value of Q-factor means - higher voltage magnification & high selectivity.  $Q = \frac{\text{Resonant freq}}{\text{BW}}$

Parallel or current Resonance



$$f_r = \frac{1}{2\pi \sqrt{LC}}$$
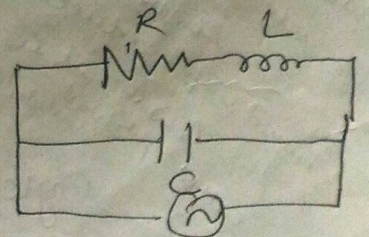
$$\text{effective impedance} = \frac{L}{RC}$$



When impedance is purely resistive, maximum in magnitude =  $L/RC$   
 This ckt is also known as rejector ckt, because at resonant freq. the line current is minimum or it almost rejects it.  
 \* Also called current resonance.

11e1 Resonance :-

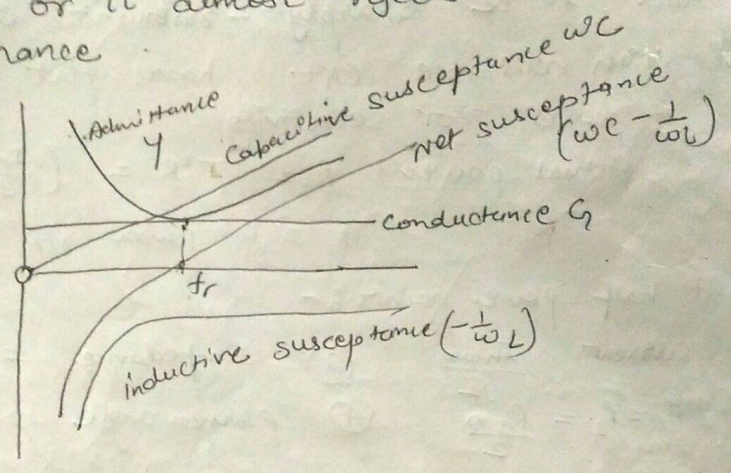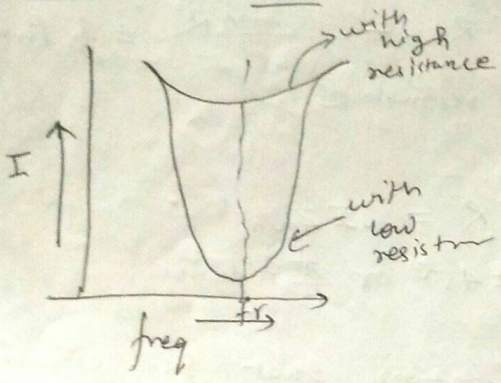

freq. lower than resonant freq. the inductive susceptance is more than capacitive susceptance. therefore line current lags behind the applied voltage.  
 for freq > resonance freq. capacitive susceptance is large so current leads the voltage.

BW Quality factor :-  $Q = \frac{X_L}{R} = \frac{2\pi f_r L}{R}$

higher the value of Q, the more selective is the tuned ckt.

- Advantages of Tuned ckt :-
- ① High selectivity
  - ② Small collector voltage
  - ③ Small power

Tuned Amplifier

Large signal = amplification of large signal at RF ~ uses class B & C operation (Class A can't be due to low efficiency)

Disadvantage :-  
 for high selectivity → high Q factor  
 Low BW  
 so Tuned amp<sup>r</sup> reduce the BW. This is called potential instability

Small signal = Amplification of small signal at R.F. uses class A

Single tuned  
 one 11e1 tuned ckt

Double tuned  
 two inductively coupled tuned ckt.  
 Ever come potential instability.