


Wave shaping Circuits :- Wave shaping is a part of signal processing where the signal waveform has to be properly shaped before amplification.

- * In this process the output may vary in shape from input because of influence of the circuit elements on the signal.
 - * Wave-shaping may be of two types →
- ① Linear wave shaping - In this, signal shape is altered by transmitting it through a linear network [network consisting of linear element such as R, L and C]. Thus R-C, R-L and R-L-C circuits are categorised as linear wave shaping circuits.
 - ② Non-linear wave shaping - In this, the shape of a signal is moderated by transmitting it through a non-linear n/w. [N/w consisting diode, transistor, vacuum tube]. The application of this kind of circuits in amplitude limiting, clipping & clamping of signals.

R-C Differentiator :- A circuit that gives an output voltage proportional to the derivative of its input.

$$\text{Output} \propto \frac{d}{dt} (\text{Input})$$

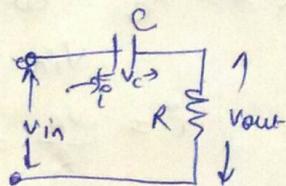The output across R will be the derivative of input V_{in} voltage.



To make R-C series circuit as a differentiator, there are conditions:-

- ① The time constant $RC \ll T$ [time period of the op signal]
- ② The value of X_C ($\frac{1}{2\pi f C}$) should not smaller than $10R$.

$$X_C \geq 10R$$

* V_{in} - i/p voltage i = instantaneous current.

Charge through capacitor $q = C V_C$ $[V_C \rightarrow \text{instantaneous voltage across capacitor}]$

$$i = \frac{dq}{dt} = \frac{d}{dt} [C V_C]$$

$$i = C \frac{dV_C}{dt}$$

$$i = C \frac{dV_{in}}{dt} \quad \text{--- (1)}$$

i.e. as $X_C \geq 10R$
 $V_C = V_{in}$

Output voltage $V_{out} = iR$

$$\Rightarrow V_{out} = RC \frac{dV_{in}}{dt}$$

Vout $\propto \frac{dV_{in}}{dt}$

Application - R-C differentiator [High pass filter] is employed to generate pulses for triggering electronic circuits such as multivibrators, flip-flops etc.

RC - Integrator - A circuit that gives an output voltage directly proportional to the integral of its i/p is known as integrating circuit.

$$\text{output} = \int \text{Input}$$

The conditions to be fulfilled for making an RC series circuit as an integrator are given below :-

- ① $RC \gg T$ [the time constant RC should be very large as compared to the time period of i/p signal]
- ② R should not smaller than 10 times the capacitive reactance

$$R \geq 10X_C \Rightarrow R \geq \frac{10}{2\pi f C}$$

* as $R \gg X_C$ so output voltage = i/p voltage [large voltage drop across R]

$$V_R = \frac{V_{in}}{R}$$


$$i = \frac{V_R}{R} = \frac{V_{in}}{R} \quad \text{--- (I)}$$

$$\text{charge across capacitor } q = \int i dt = \frac{1}{R} \int V_{in} dt \quad \text{(from eqn I)}$$

$$\text{output } V_{out} = \frac{q}{C} = \frac{1}{CR} \int V_{in} dt \quad \text{--- (II) (from eqn II)}$$


$$V_{out} \propto \int V_{in} dt$$

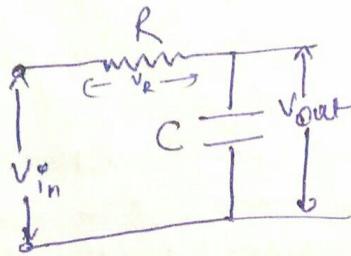Application - R-C Integrator (low pass filter) used in generation of triangular and ramp waveforms. It also used in discrimination b/w pulses of different lengths



R-L differentiator :- The output across the inductor is proportional to the derivative of I/P voltage.

$$V_{out} \propto \frac{d}{dt} V_{in}$$

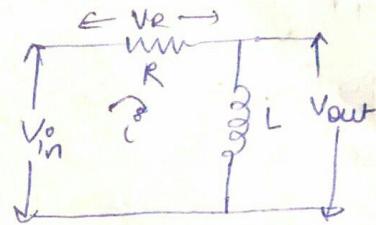

To make R-L differentiator, there are conditions:-

- (i) The time constant ($\tau = \frac{L}{R}$) << T
- (ii) The value of $X_L \leq 10R$ ($X_L = 2\pi f$)

* as the value of R is very large so voltage drop across it $V_R = 0$

$$V_{in} = \cancel{V_R} \quad \text{the instantaneous current } i = \frac{V_R}{R} = \frac{V_{in}}{R} \quad \text{--- (1)}$$

$$\text{voltage across inductor } V_{out} = L \cancel{\frac{di}{dt}}$$

$$V_{out} = L \frac{d}{dt} \left(\frac{V_{in}}{R} \right) \text{ from eq (1)}$$


$$V_{out} = \left(\frac{L}{R} \right) \frac{dV_{in}}{dt}$$

$$V_{out} \propto \frac{d}{dt} V_{in}$$

Application - To generate a time delay

R-L integrator :- The output across the resistor is directly proportional to the integral of input voltage

$$V_{out} \propto \int V_{in}$$

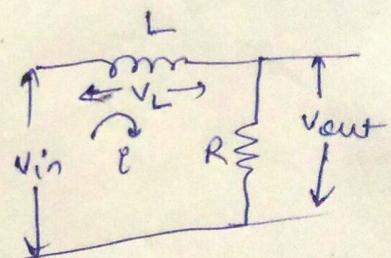

Condition:-

- (i) Time constant $T \gg T$

- (ii) $X_L \geq 10R$

$$\text{Current through inductor } i = \frac{1}{L} \int V_L dt \quad \text{--- (2)}$$

$$\text{Output across R} \quad V_{out} = iR$$

$$V_{out} = \frac{R}{L} \int V_L dt \quad \text{for eq (2)} \quad V_L = V_{in}$$

$$V_{out} \propto \int V_{in}$$

Non-linear wave shaping circuits :-


① Clipping circuits:- A wave shaping circuit which controls the shape of the output waveform by removing or clipping a portion of the applied wave is known as clipping CKT. These circuits used in radars, digital computers and other electronic system.

clippers may be - ① Positive clippers ② Negative clippers
 ③ Beased clippers ④ Combination clippers

(A) Positive clippers - The clipper which removes the positive half cycle of the I/P voltage.

(i) Positive series clipper circuit →

In this diode is in series with R_L .

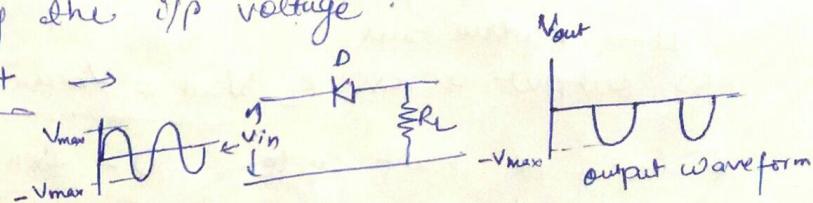


* when V_{in} has +ve half cycle the diode (D) is in reverse bias so $V_{out} = 0$

* when V_{in} has -ve half cycle the diode (D) is in forward bias so $V_{out} = -V_{max}$

(ii) Positive shunt clipper circuit →

In this diode is in parallel with R_L .

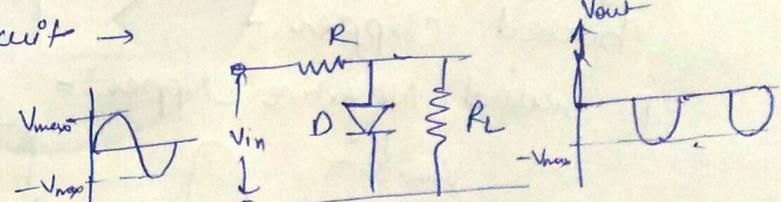

* when V_{in} has +ve half cycle the diode D is in forward bias so all voltage drop across diode, the output of R_L is zero $\boxed{V_{out} = 0}$


* when V_{in} has -ve half cycle the diode D is in reverse bias so all voltage drop across R_L .

$$\boxed{V_{out} = -V_{max}}$$

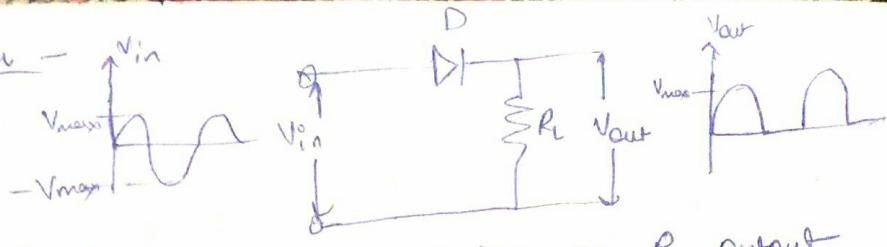(B) Negative clippers:- The clipper which removes the negative half cycle of the I/P voltage.

① Negative series clipper :-

- for +ve half cycle diode V_{max}
D is in forward bias
so $V_{out} = V_{max}$




- * for -ve half cycle diode D is in reverse bias so R_L output
 $V_{out} = 0$

② Negative shunt clipper :-

- for +ve half cycle
D → Reverse bias


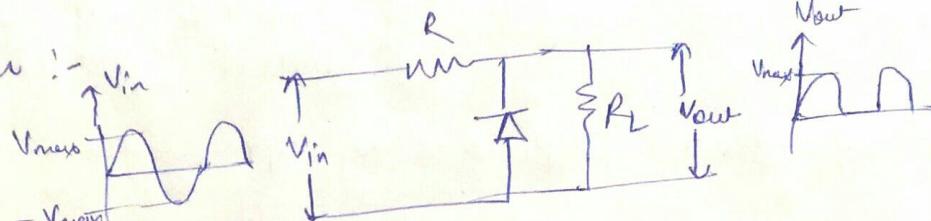
$$\text{so output across } R_L \quad V_{out} = V_{max}$$



- * for -ve half cycle D → forward bias so all voltage drop across diode & the output voltage across $R_L = 0$

(c) Biased clipper :- Sometimes it is desired to remove a small portion of positive or negative half cycle of the signal voltage. So at this condition we use biased clipper =

iii Biased Negative clipper :-

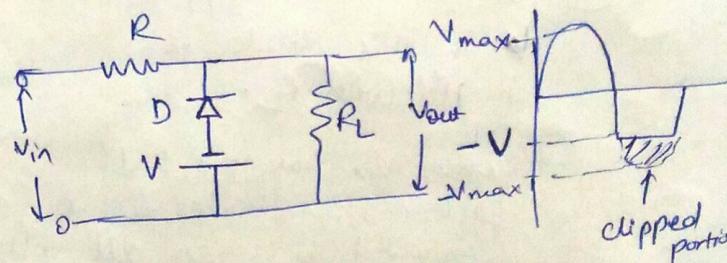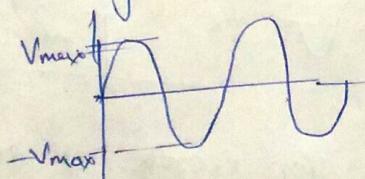


- * for +ve half cycle - The diode is in reverse bias
so voltage drop across R_L $V_{out} = V_{max}$


- * for -ve half cycle → The diode is in forward bias

$$-V - V_{out} = 0$$

$$V_{out} = -V$$

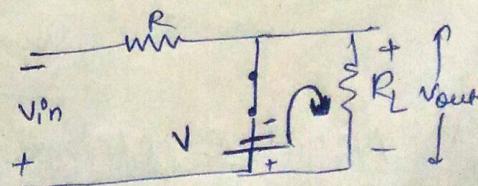

⑪ Biased Positive Clipper \rightarrow

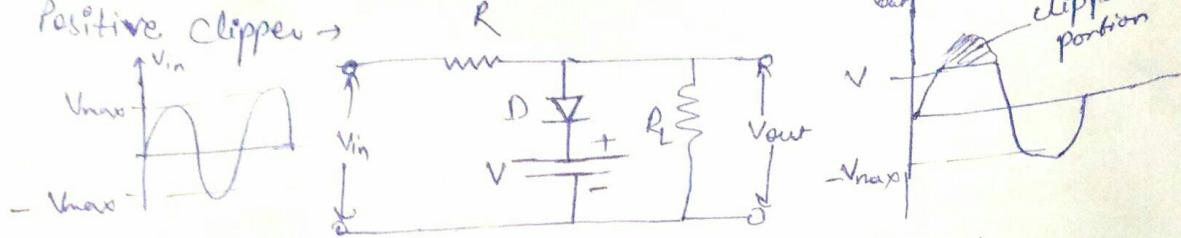


* for +ve half cycle \rightarrow diode D is in forward biased

$$V - V_{out} = 0$$




$$\boxed{V_{out} = V}$$

* for -ve half cycle \rightarrow D is in reverse bias, all voltage drop across R_L

$$\boxed{V_{out} = -V_{max}}$$

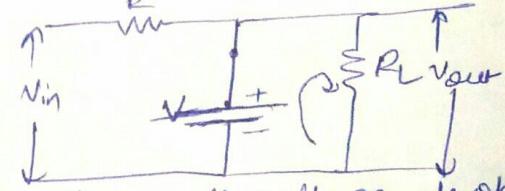

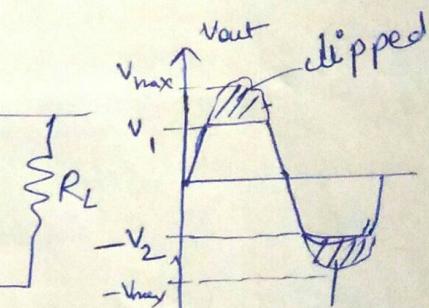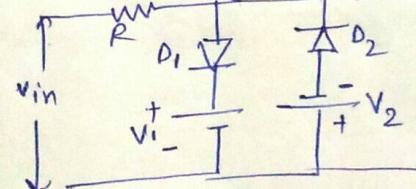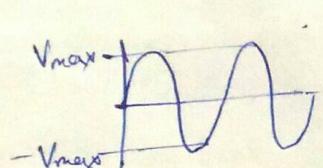
⑫ Combination clipper \rightarrow when a portion of both +ve & -ve of each half cycle of I/P is to be clipped combination clipper is employed.



* when +ve half cycle of V_{in} \rightarrow The diode D_1 is in forward bias while D_2 is in reverse bias so \rightarrow

$$V_1 - V_{out} = 0$$

$$\boxed{V_{out} = V_1}$$

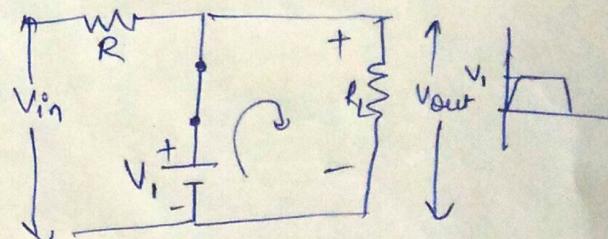

* when -ve half cycle of V_{in} occurs \rightarrow The diode D_1 is off (R.B.) & D_2 is ON (forward bias)

$$-V_2 - V_{out} = 0$$

$$\boxed{V_{out} = -V_2}$$

